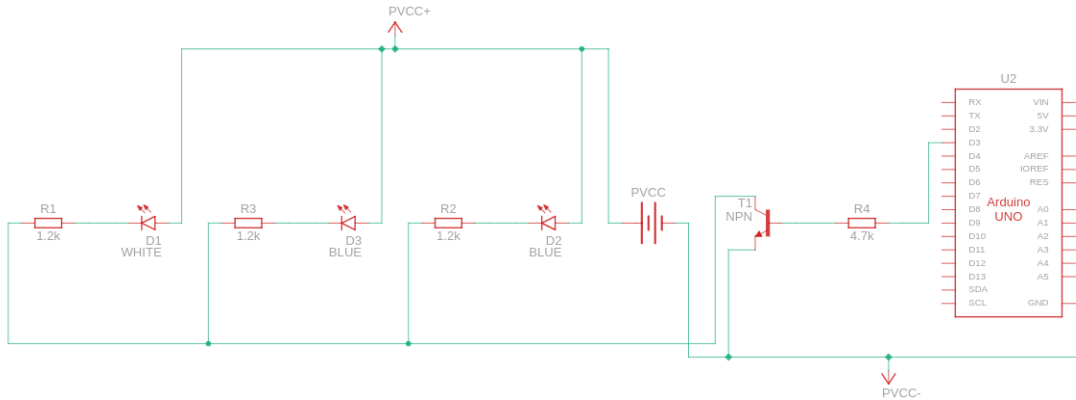
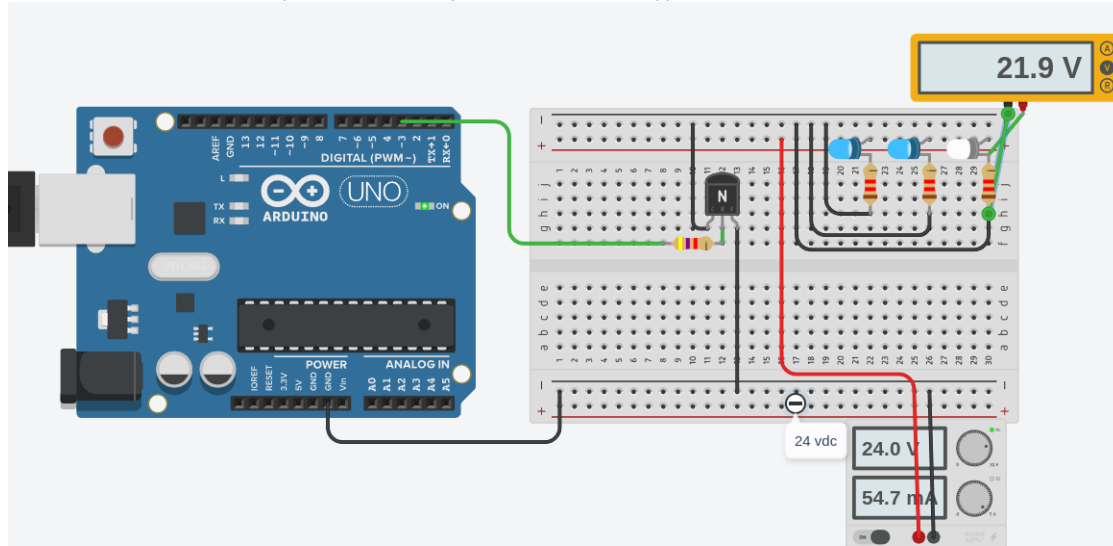


# NPN Transistor

Below I'm calculating required resistance between microcontroller and Base of transistor using: 2N222A NPN Transistor and esp8266(NodeMCU1.0(ESP-12E Module)) and arduino IDE.



Calculate resistor at base of transistor (B)

- Calculate total current through transistors Collector pin  $I_C$ : 3-led branches @  $18.2_{mA} = 54.7_{mA}$  (This includes a .2 voltage drop, transistor Collector(C) to Emitter(E))
- from data sheet we see  $\beta$  or  $h_{FE}$  range of 40-300 I'll use **150**
- Calculate amount of current to transistor Base by:  $\frac{I_{Collector}}{h_{FE}} = \frac{54.7_{mA}}{150} = .36_{mA}$
- Calculate resistor to Base(B) of transistor (Note voltage drop of .7 between transistor B and E,  $V_{BE}$ )

$$R_B = \frac{V_{GPIOin} - V_{BE}}{I_B} = \frac{3v - 0.7v}{.36_{mA}} = 6389\Omega$$

- reduce resistance, by  $\sim \frac{1}{2}$  to make sure transistor switches, in this example 4.7K resistor